

NATIONAL RADIO ASTRONOMY OBSERVATORY  
Green Bank, West Virginia

Electronics Division Internal Report No. 138

UNIVERSAL VOLTAGE REGULATOR

Don Q. Morris

FEBRUARY 1974

NUMBER OF COPIES: 150



UNIVERSAL VOLTAGE REGULATOR

Don Q. Morris

TABLE OF CONTENTS

	<u>Page</u>
<u>Introduction</u> .....	1
<u>General Description</u> .....	1
<u>Applications</u> .....	2
<u>Options</u> .....	5
1. Remote voltage control, $V_L \leq 30$ V .....	5
2. Remote sensing .....	5
3. Remote metering .....	5
4. Remote shutdown .....	5
5. Thermal shutdown .....	6
6. Short circuit shutdown, manual reset .....	6
7. Fault indication .....	7
8. Overvoltage protection .....	7

LIST OF FIGURES

1	Packaging of regulator and O/V protection cards .....	9
2	Regulator card and panel .....	10
3	Overvoltage protection card and panel .....	10
4	Low current regulator card .....	11
5	Regulator card with 13 W heatsink .....	12
6	Regulator card assembly .....	13
7	Overvoltage protection card assembly .....	14
8	Application and option chart .....	15
9	Regulator circuit diagram .....	16
10	Overvoltage protection circuit diagram .....	17
11	Regulator card layout .....	18
12	Overvoltage protection card layout .....	19
13	Heatsink/panel for regulator card .....	20
14	13 W heatsink for regulator card .....	21
15	Heatsink/panel for overvoltage protection card .....	22



## UNIVERSAL VOLTAGE REGULATOR

Don Q. Morris

### Introduction

The power supply components to be described in this report were originally designed to power and protect Gunn diode oscillators having critical operating parameters. However, they should be suitable for a wide variety of applications due to the many electrical and mechanical options incorporated.

### General Description

1. The voltage regulator card is 2.75 inches wide by 3.43 inches long, to be used with 15 pin edge connector, Cinch 50-30A-30. The associated panel and/or heatsink is designed to allow side by side placement of cards on one inch centers. The regulator circuit is designed around the Motorola integrated circuit voltage regulator MC 1469R, with the necessary flexibility of connections to satisfy most voltage regulator needs. It is especially useful when multiple output voltages are desired without the expense and space required for separate regulated supplies.

2. The overvoltage protection card is the same size and uses the same type connector as the regulator card. The heatsink and panel (Figure 15) is designed for side by side mounting with the regulator card using heatsink/panel, Figure 13. The handles used are H. H. Smith #1641.

The basic circuit is a crowbar with adjustable trip point. When the voltage across the load exceeds a predetermined level set by R2, Q1 triggers, driving the SCR Q2 into full conduction within 0.5  $\mu$ sec. When Q2 is conducting the output is shorted, blowing fuse F1.

The trip point bias is derived from the unregulated supply to permit a wide range of adjustment of trip point.

### Applications

1. Basic regulator for output voltage of 5 to 30 V and load current to 400 mA.

Use Thermalloy 6168B heatsink or Figure 13 heatsink and panel. Maximum heat dissipation with either is about 3.5 watts in still air.

See Figure 8 chart for components and jumpers required. Refer to Figures 6 and 9 for connections and locations.

F2, 0.5A

$R1 + R2 \approx (2 \text{ V out} - 7) \text{ K}\Omega$ . R2 may be on remote panel.

R13, select for about 5 mA at desired V out.

R17 = 1.5  $\Omega$  1/2 W.

2. Basic regulator for output voltage of 5 to 30 V and load current to 1.2 amp.

Use Figure 13 heatsink/panel for on-board control and up to 3.5 watts dissipation. For power dissipation up to 13 watts use Figure 14 heatsink and remote controls. If more than 13 watts dissipation is required the heatsink may be fan cooled or external power transistor and heatsink may be used, as in Basic Regulator No. 3.

See Figure 8 chart for components and jumpers required. Refer to Figure 6 and Figure 9 for connections and locations.

F1 - 2A

F2 - .5 A

$R1 + R2 \approx (2 \text{ V out} - 7) \text{ K}\Omega$

R13 - select for about 5 mA at desired V out.

R14 - 100  $\Omega$

R17 - 0.5  $\Omega$ , 1 W.

3. Basic regulator for output voltage of 5 to 30 V and load current above 1.0 amp using external pass transistor.

Use Figure 13 heatsink/panel for on-board control or Figure 14 heatsink with remote control.

See Figure 8 chart for components and jumpers required. Refer to Figure 9 for connections and Figure 6 for locations.

F1, 2A

F2, .5 A

R1 + R2 (2 V out - 7) K


R13, select for about 5 mA at desired V out

R14, 100

R15, 100

R17 - use external current limiting resistor =  $0.6/I$  and sufficient power rating unless using short circuit shutdown option. With this option a resistor of lower power rating may be used on the board since it does not have time to heat up before regulator shutdown.

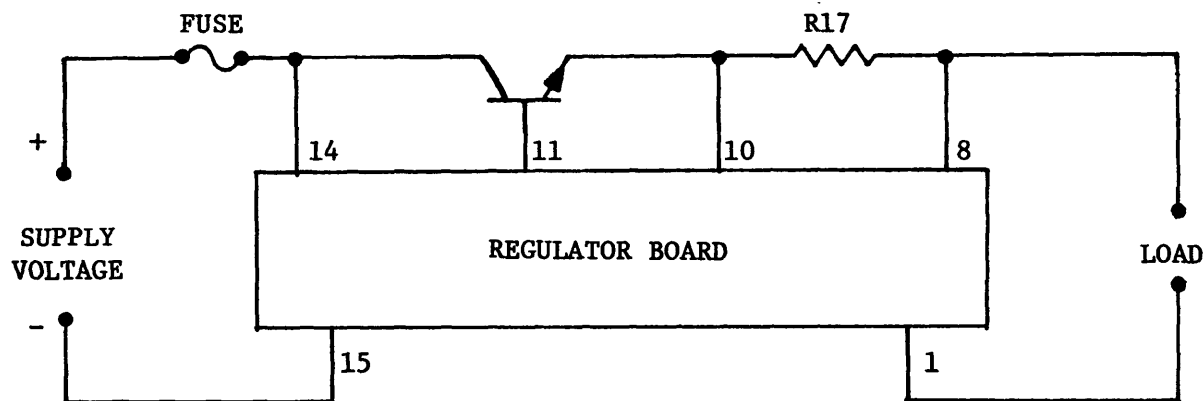Connect regulator board and external pass transistor as shown:



4. Basic regulator for output voltage of 30 to 70 V and load current to 1.0 amp.

Use Figure 8 chart for components and jumpers required. Refer to Figure 9 for connections and Figure 6 for locations.

F1, 2A

F2, .5A

Q3, substitute 2N 5192 (80 V rating)

D2, 1N 4001

VR2 select to provide approximately 30 V at pin 3 of MC 1469R

VR4 same as VR2

R1, 43K, R3, 6.8 K, omit R2


R10, 2K

Select R13, R18, and external pot to provide approximately 25 V at arm of pot with 1 mA thru divider.

R16, 4.7 K

R17, 0.5 ohm

Connect external components as shown:

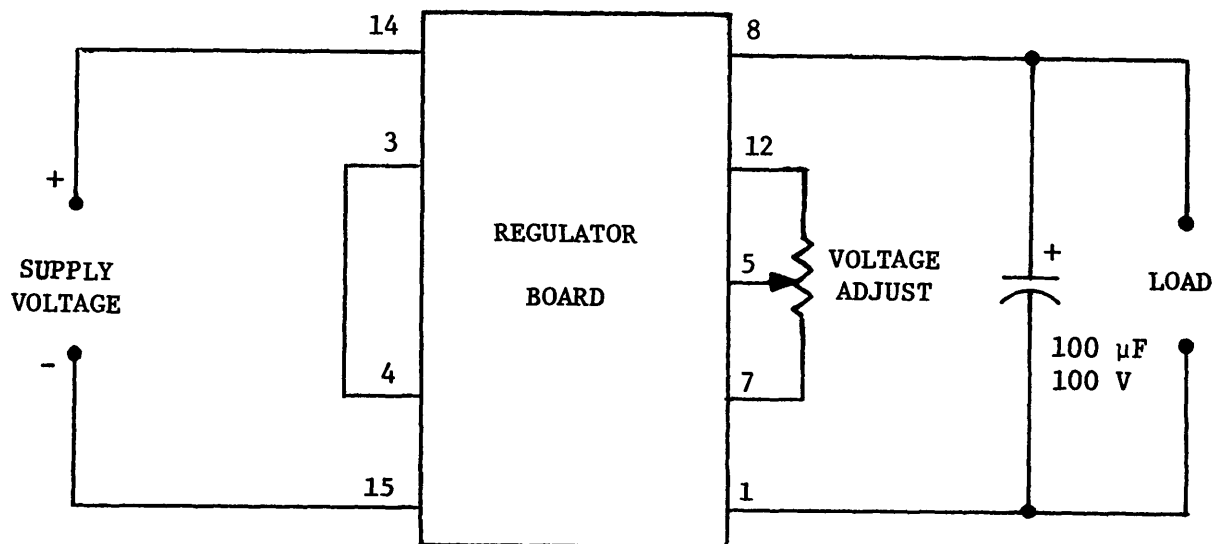



Options


1. Remote voltage control,  $V_L \leq 30$  V.

Omit potentiometer R2 and connect an equivalent remote potentiometer to terminals 3 and 4 of regulator board.

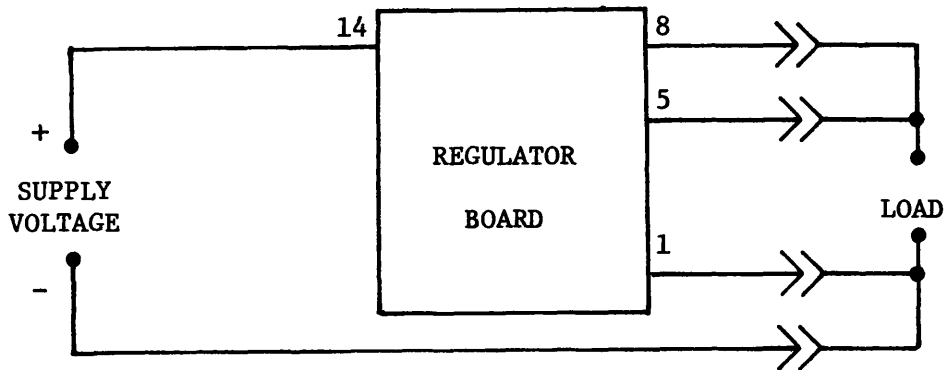2. Remote sensing.

Omit J10 and J11 on regulator board and add J9.

Make external connections to regulator board as shows:



3. Remote metering.

If desired to monitor regulated voltage and load current over a long cable, the cable drop may be minimized by using very low current meters with series multiplier resistors. R18 may be used as the voltmeter multiplier.

The load current may be monitored by metering the voltage drop across R17 with meter current limited by R19.

4. Remote shutdown.

The regulator may be put in a standby condition with zero output by applying a positive voltage in excess of 1.2 V DC to terminal 6 on the regulator card. R9 should be selected to limit current to less than 10 mA. One mA is sufficient to shut down the regulator.

5. Thermal shutdown.

The voltage regulator 1C, and Q3 as well, may be protected from destruction due to excessively high junction temperatures by the addition of VR1, R4, R7, and R8, which are used to provide a fixed voltage of approximately 1 V at pin 2 of the regulator 1C. This will cause the regulator to shutdown when the temperature of the chip exceeds approximately 130°C, due to the negative temperature coefficient of the diode in series with pin 2 and the base-emitter junction of the shutdown transistor, both in the regulator 1C.

VR1 = 1N4733A, R4 = 100 (Vs-5), R7 = 2.0 K, R8 = 560 ohm.

6. Short circuit shutdown, manual reset.

This option will latch the regulator into shutdown condition when the voltage at junction of R12 and R13 drops more than 0.5 volt below the voltage at junction of R5 and R7. Regulator will remain shutdown until supply voltage to R4 is temporarily removed by means of S1 or remotely with a normally closed switch between Vs and terminal 2 of board. C1 delays initial voltage rise at anode of Q2, preventing shutdown at initial turn on.


S1 N-C PUSHBUTTON, Grayhill 30-2  
R4 Vs - 5/.015  
VR1 1N4733A  
C1 100  $\mu$ F, 6 V  
C2 .005  $\mu$ F  
R5 2.0 K  
R11 820 K  
R12 } Select to provide 5 V at junction of R12  
R13 } and R13 at normal output voltage  
Q2 2N6027 programmable unijunction

7. Fault indication.

A fault condition indication may be obtained whenever the regulator output voltage drops below normal with proper supply voltage present by use of PL1, D1, and VR3. PL1 is a 5 V Eldema lamp, which may be on the regulator board when heat-sink/panel, Figure 13, is used, or connected to terminals 2 and 13 if remote indication is desired. D1 is a 1N4002 and serves to isolate the regulator outputs from each other when multiple regulators are connected to a common fault indicator. VR3 is a 1W zener diode; its zener voltage should be approximately  $V_s - (V_s - V_L) - 3$ .

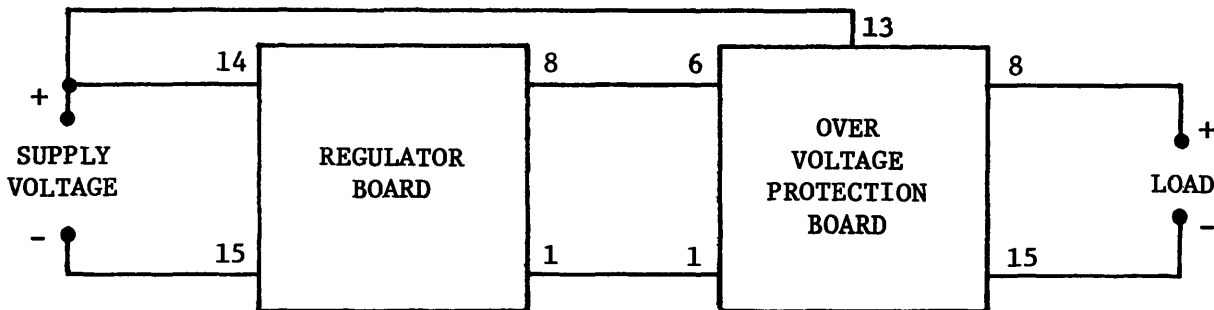8. Overvoltage protection.

Overvoltage protection for the load may be provided by use of a separate over voltage protection board PC2-490-4, together with short circuit shutdown and fault indication options on the regulator board. With this arrangement, when an overvoltage condition occurs and the SCR on the overvoltage protection card fires, a short circuit appears at the output of the regulator card and the regulator is shut down before the fuse can blow. If the regulator transistor should short, the SCR will protect the load from overvoltage until the fuse blows. The regulator and overvoltage protection cards should be interconnected as follows:



8. Overvoltage protection (continued):

The following parts are required for the overvoltage protection board:

- (1) PC board PC2-490-4
- (1) Heatsink/panel, Figure 15
- (1) Handle, H. H. Smith #1641
- (1) Fuse holder, Littlefuse #281002
- (1) Fuse, F1, Littlefuse Series 273.000
- (3) Tip jacks, H. H. Smith #1501 or similar
- (1) 5 K potentiometer, R2, Beckman 55LR5K with 55BW bushing mount
- (1) Diode D1, 1N4002
- (1) Zener diode VR1,  $V_z \geq V_L$
- (1) Resistor R1 = 60 ( $V_s - V_z$ )
- (1) Resistor R3 = 5 K
- (1) Resistor R4 = 1 megohm
- (1) Resistor R5 = 100 ohm
- (1) Capacitor, electrolytic, C1 = 10  $\mu$ F at W.V. >  $V_s$
- (1) Capacitor, disc, C2 = .005  $\mu$ F
- (1) Programmable unijunction transistor Q1 = 2N6027
- (1) Silicon controlled rectifier Q2 = 2N4443 (UPTO 8A)

Refer to Figure 6 for component layout and Figure 9 for circuit diagram.

When setting up the trip point, adjust R2 to set voltage at VTP to 0.6 V below desired maximum voltage at  $V_L$ .

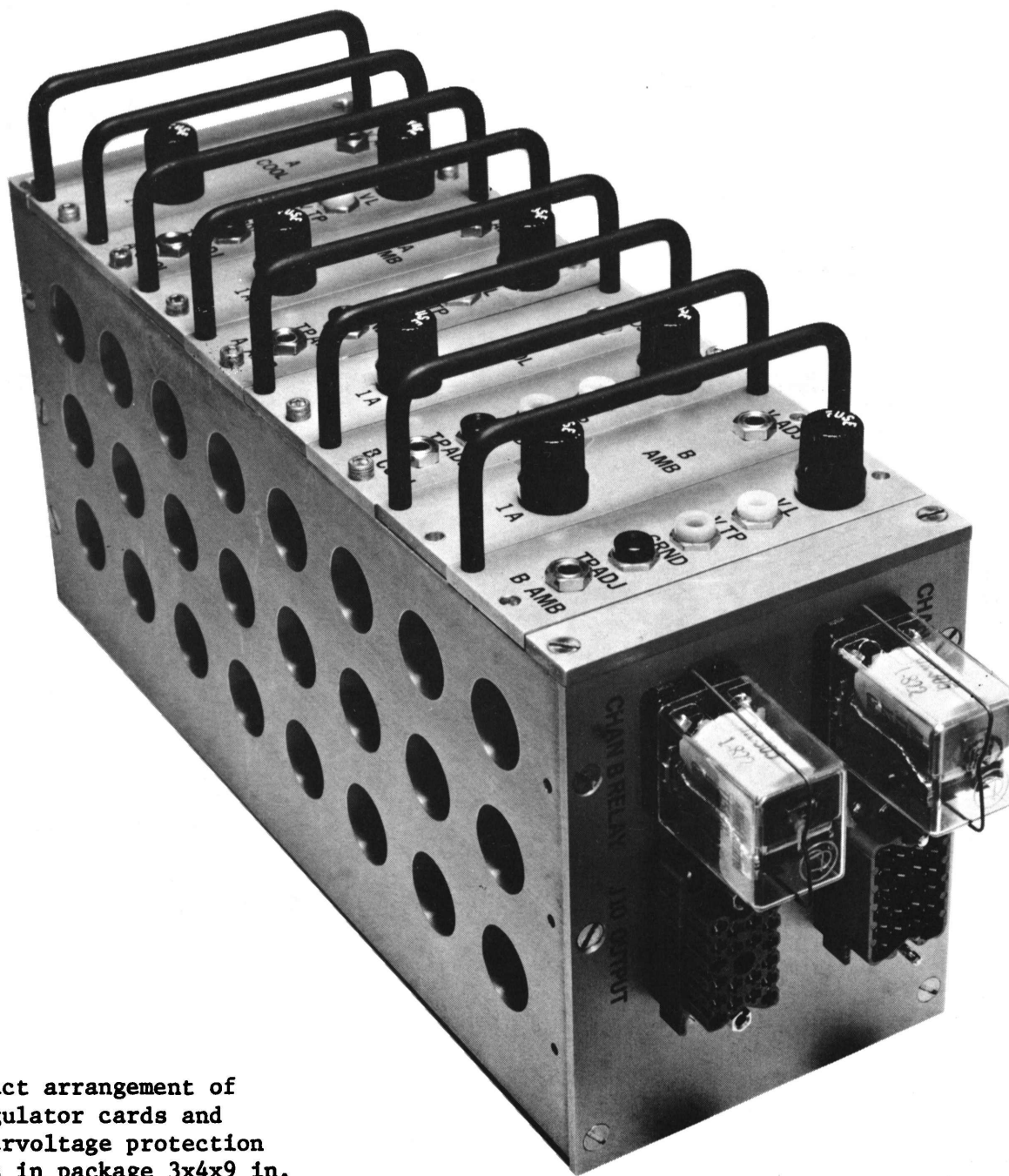


Figure 1 — Compact arrangement of  
4 regulator cards and  
4 overvoltage protection  
cards in package 3x4x9 in.

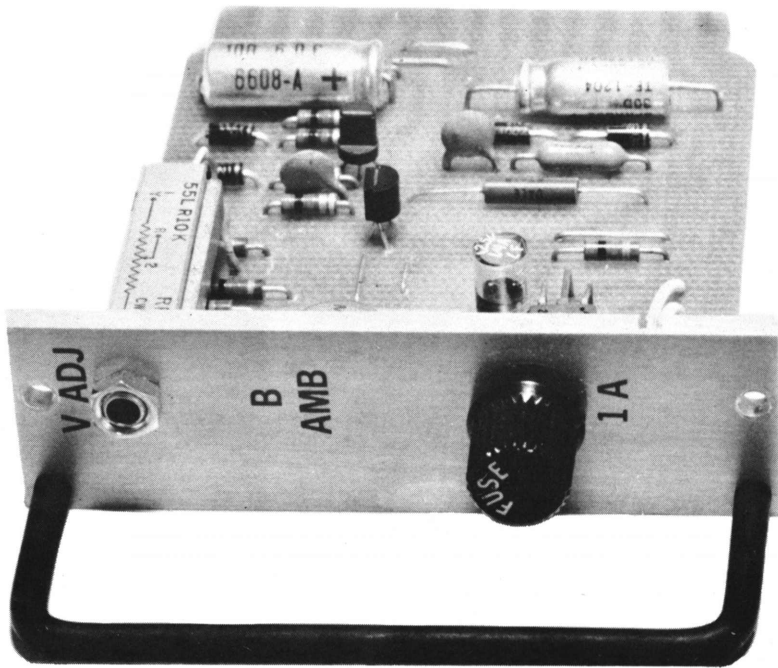


Figure 2 - Voltage regulator card with Fig. 13 panel and heatsink, and handle.

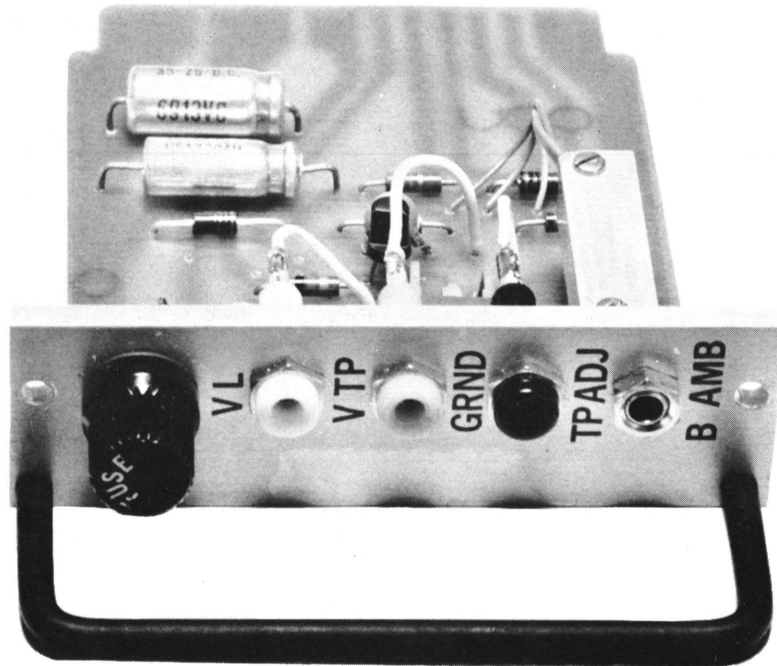


Figure 3 - Overvoltage protection card with Fig. 15 as panel/heatsink with handle.

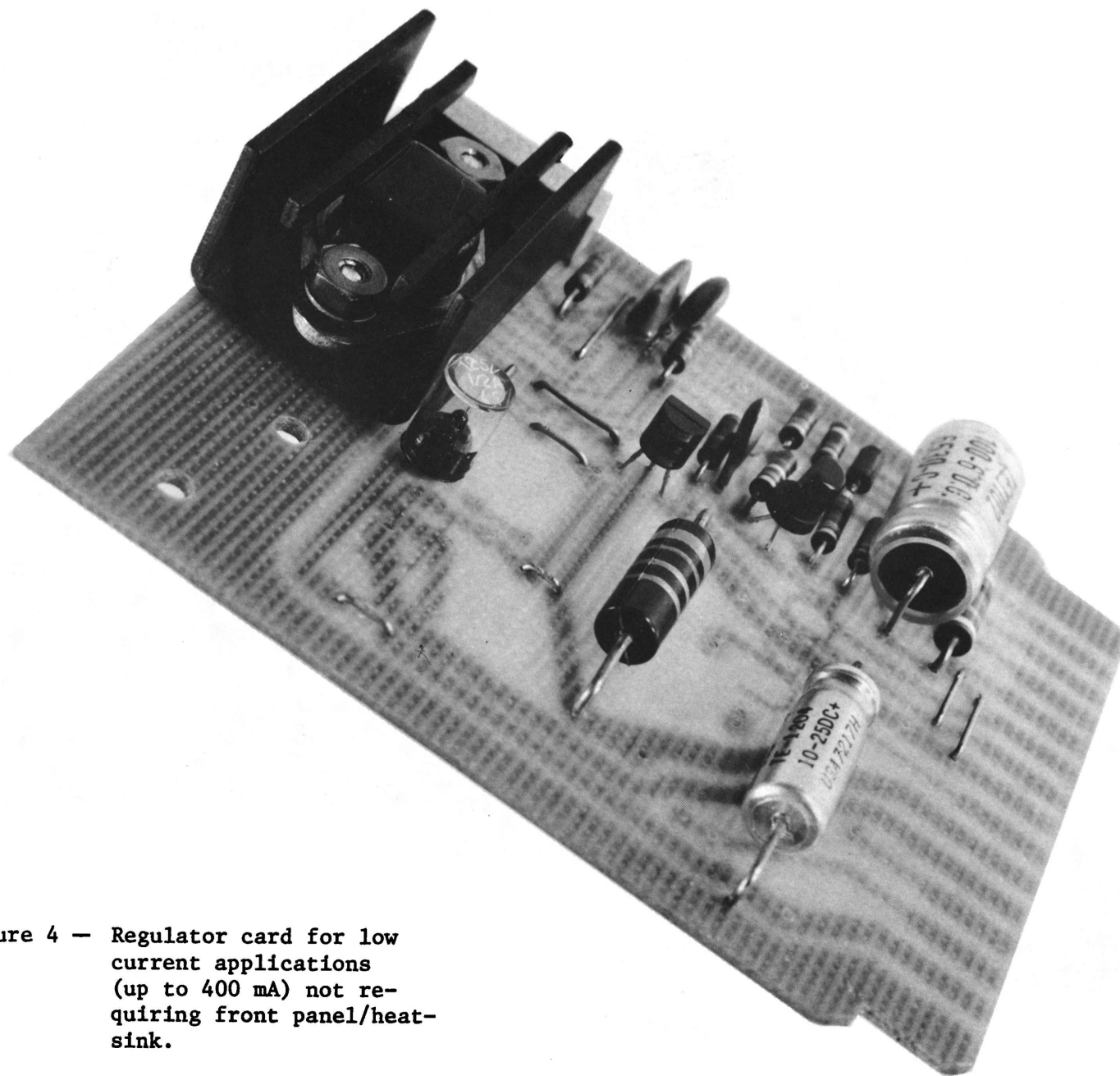


Figure 4 — Regulator card for low current applications (up to 400 mA) not requiring front panel/heat-sink.

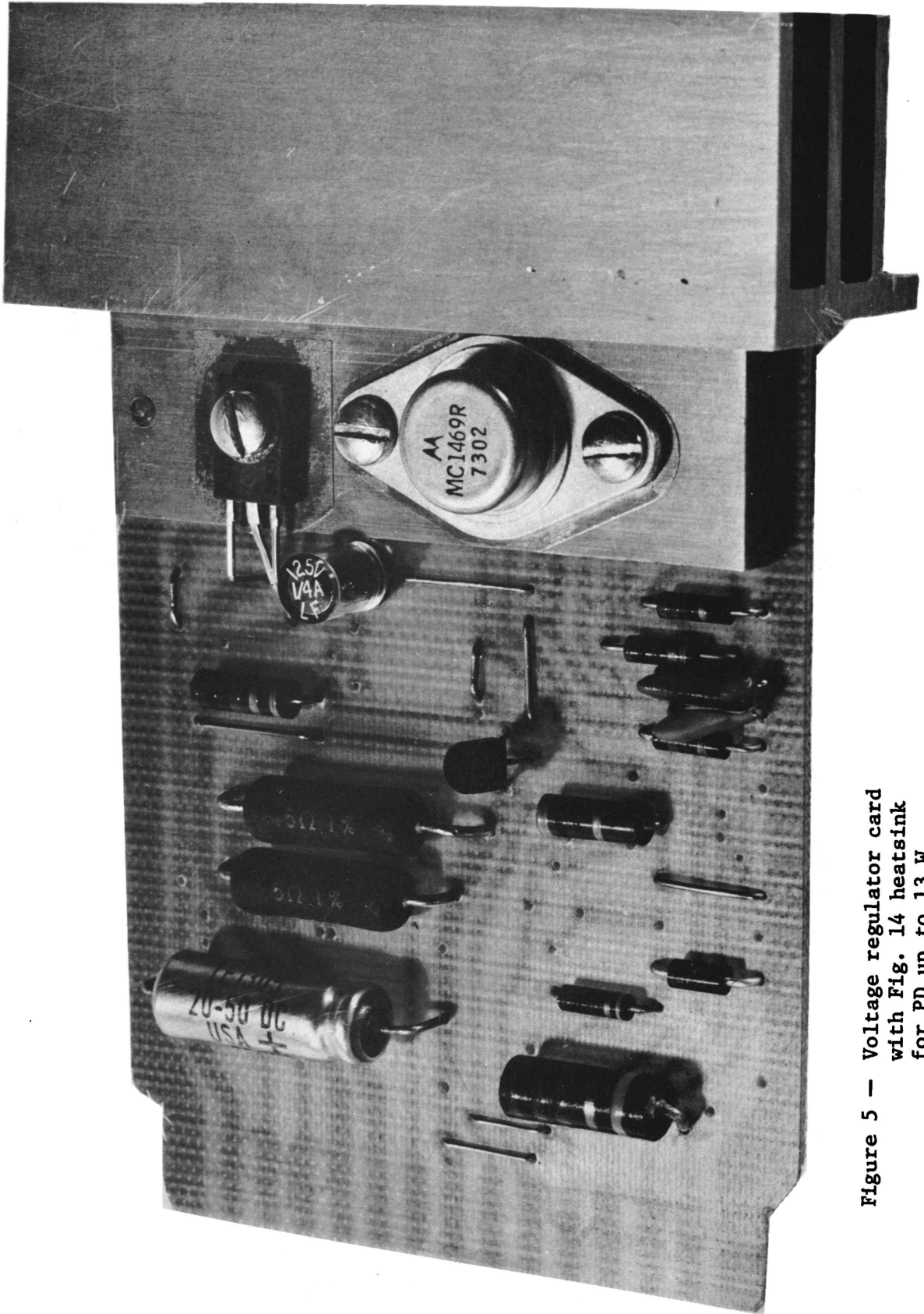


Figure 5 - Voltage regulator card with Fig. 14 heatsink for PD up to 13 W.



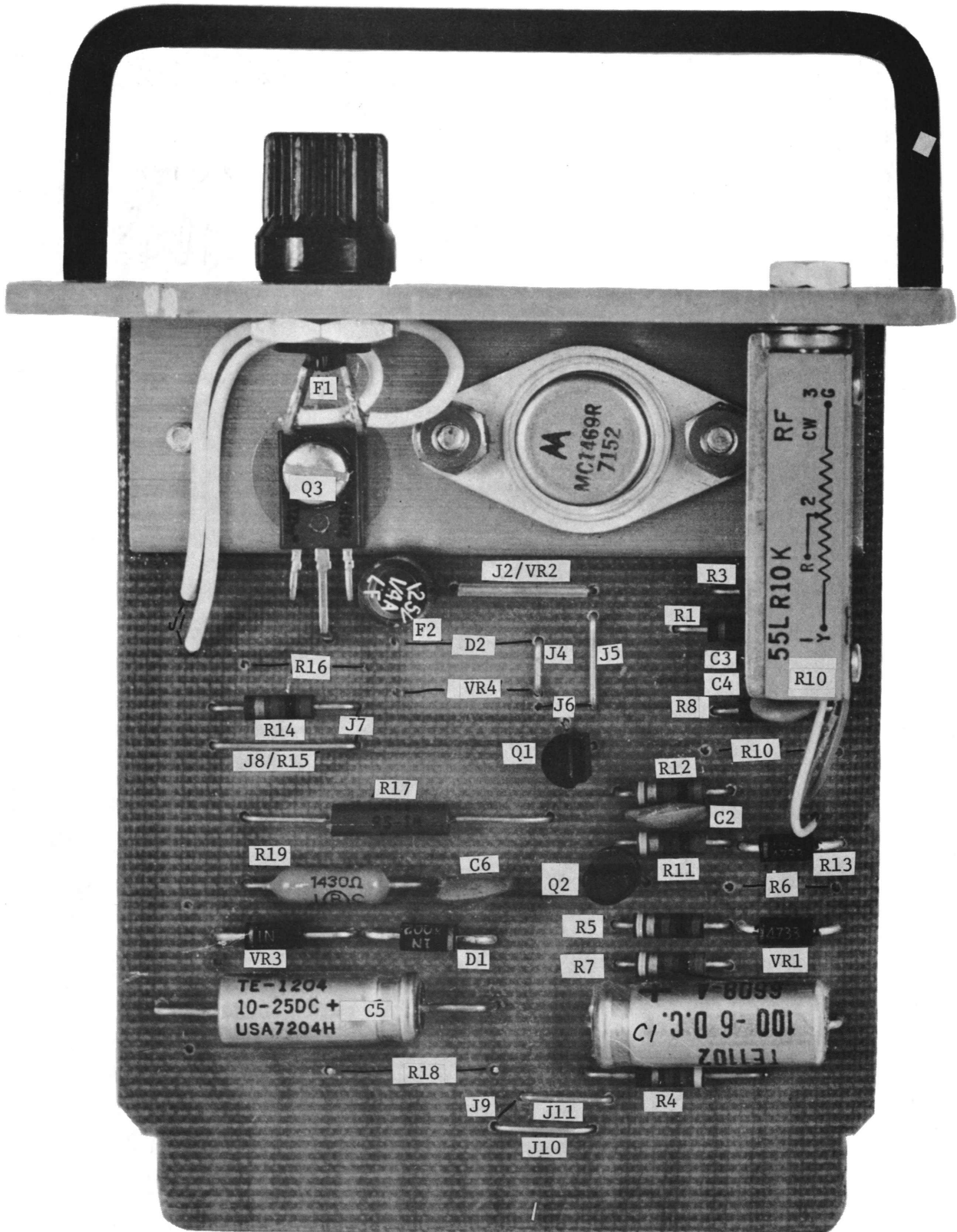


Figure 6 — Voltage regulator card assembly

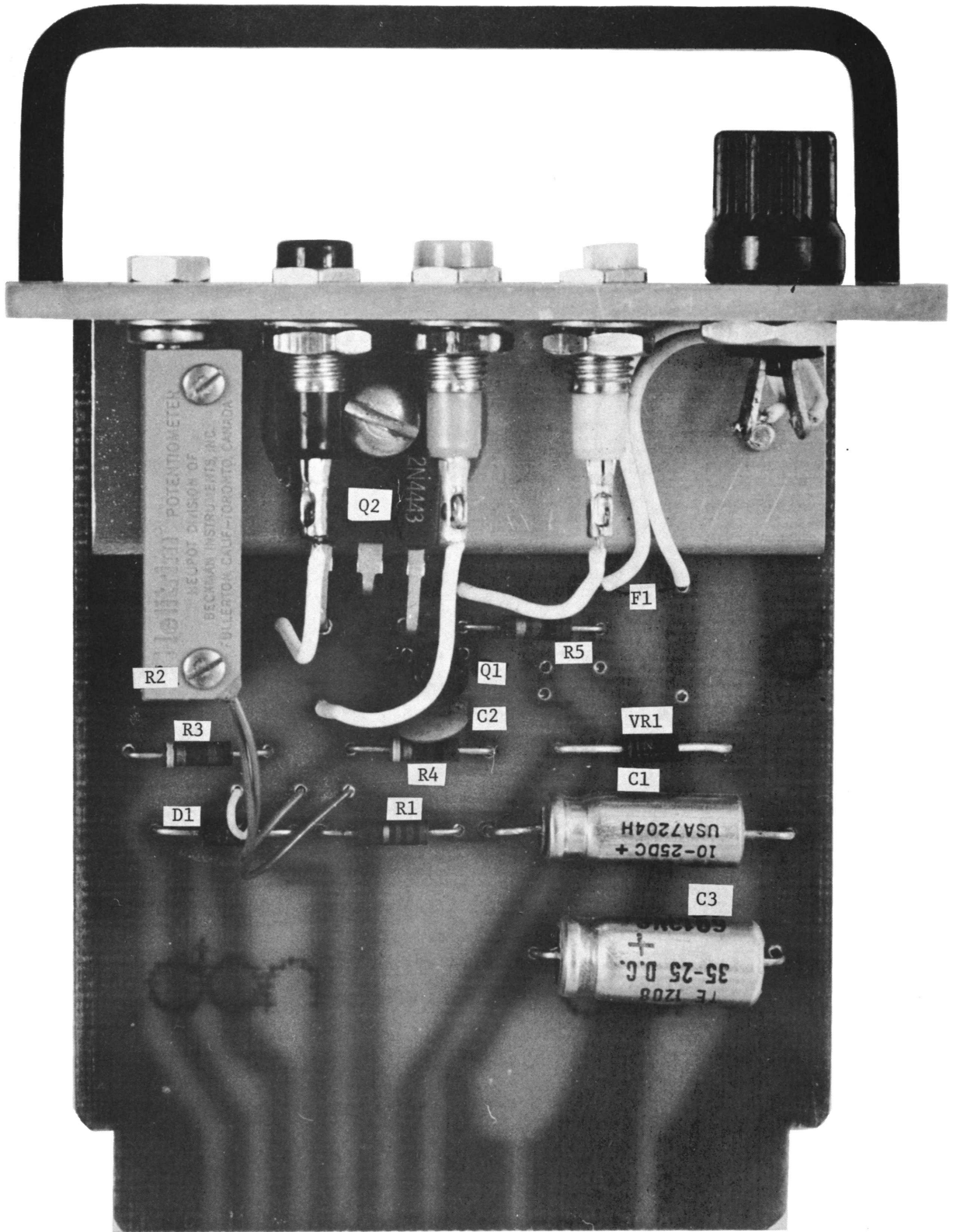


Figure 7 — Overvoltage protection card assembly




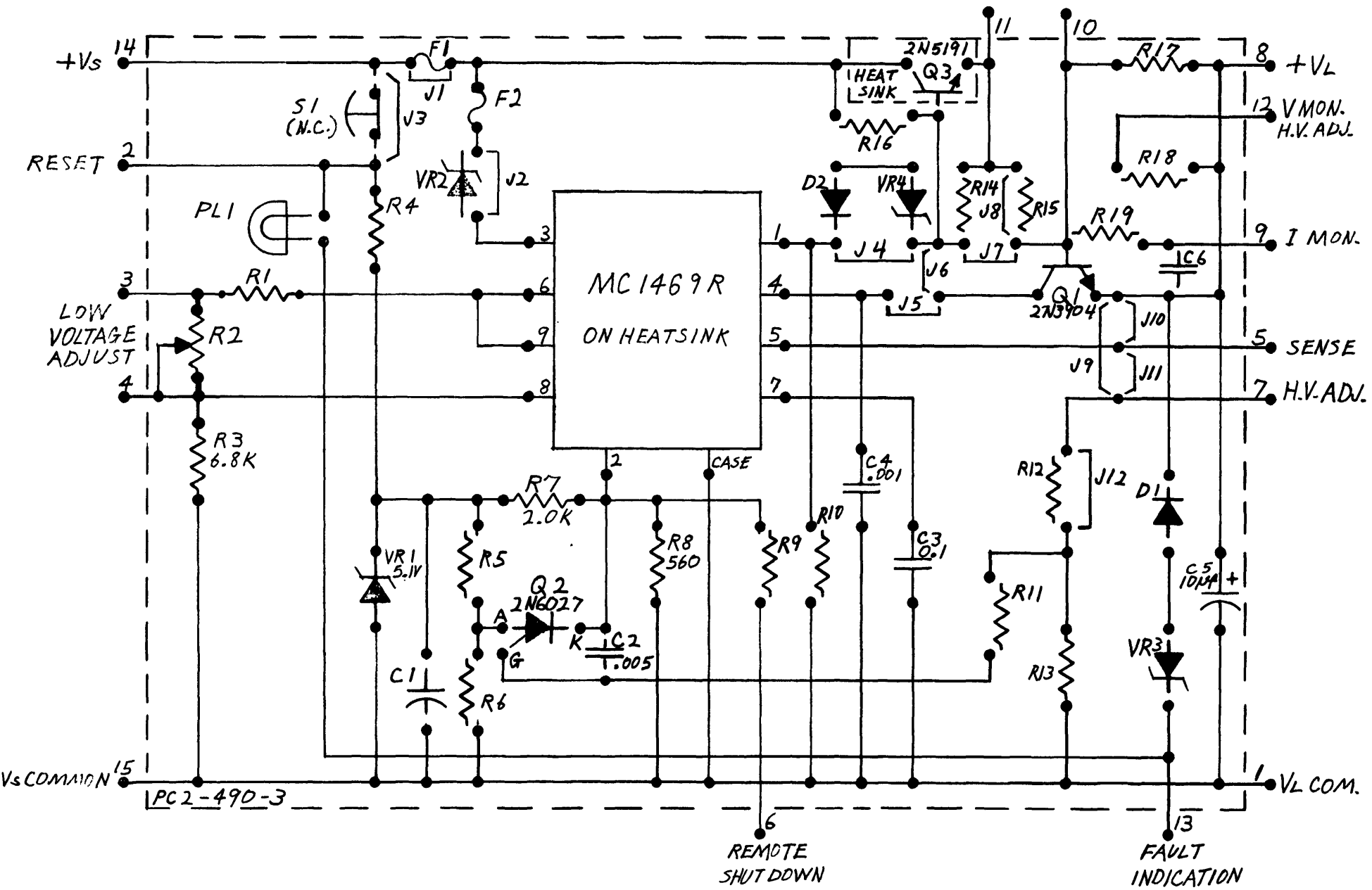


Figure 9 - Regulator Circuit Diagram

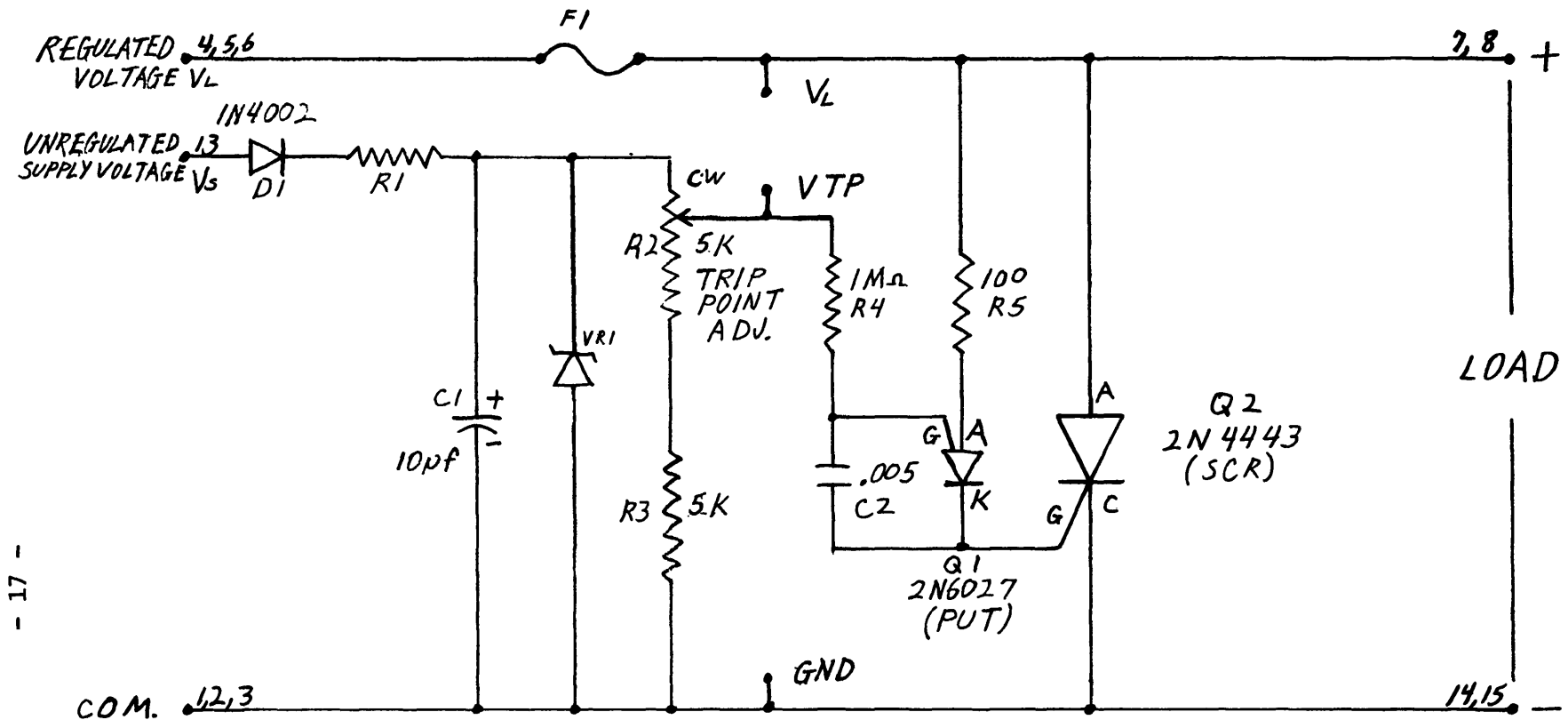

- 17 -

- NOTES:
1.  $D1$  &  $C1$  PREVENT FALSE TRIGGERING FROM NEG. TRANSIENTS ON 12V BUS.
  2. ADJUST  $R2$  TO SET VOLTAGE AT  $VTP$  TO 0.6V BELOW DESIRED TRIP POINT.
  3. SCR IS FULL ON WITHIN 0.5 $\mu$ SEC AFTER TRIP POINT IS REACHED.

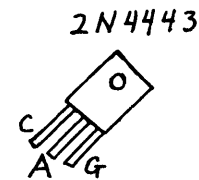
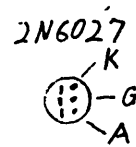


Figure 10 - Overvoltage Protection Circuit Diagram


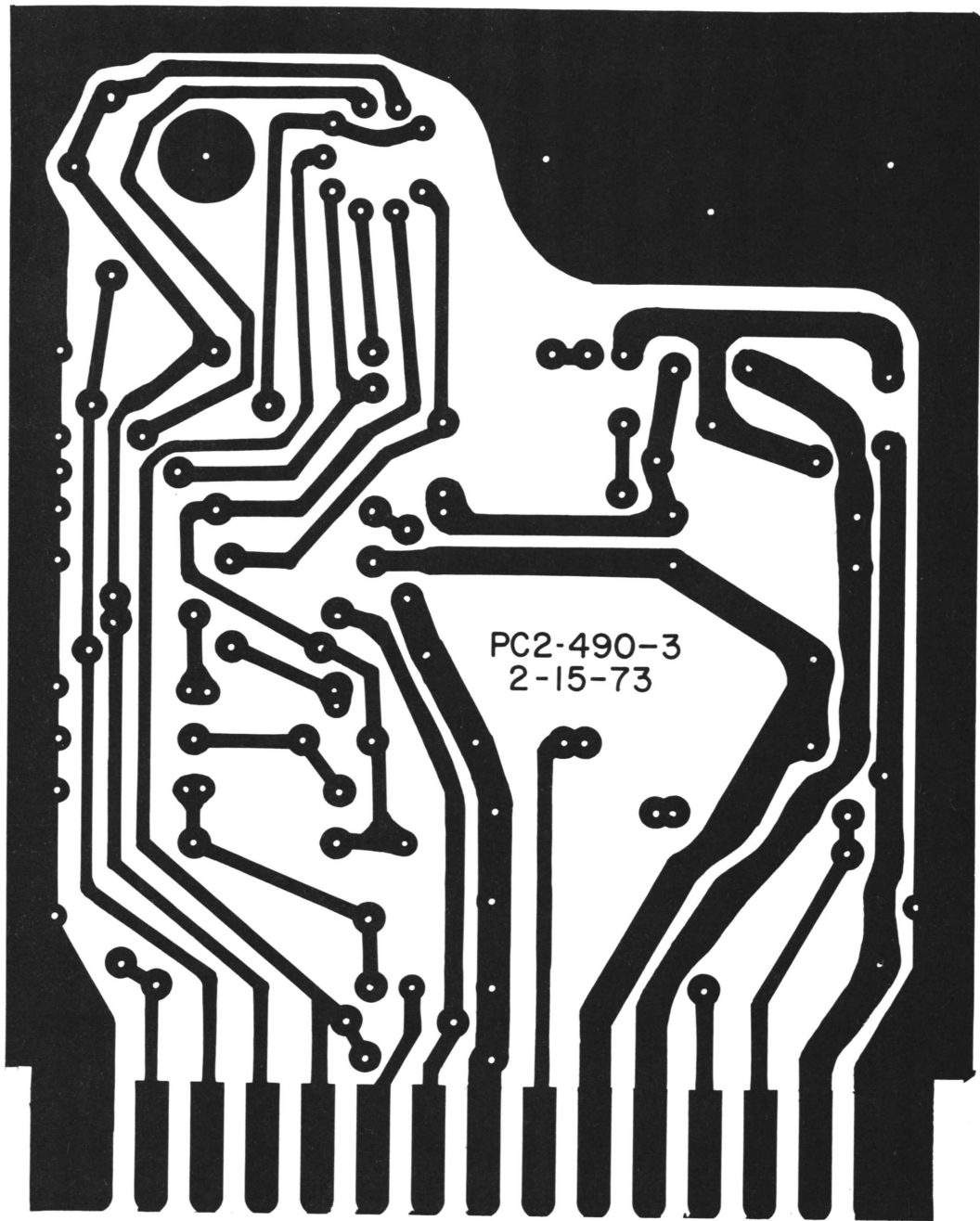


Figure 11 - Voltage Regulator Card Layout

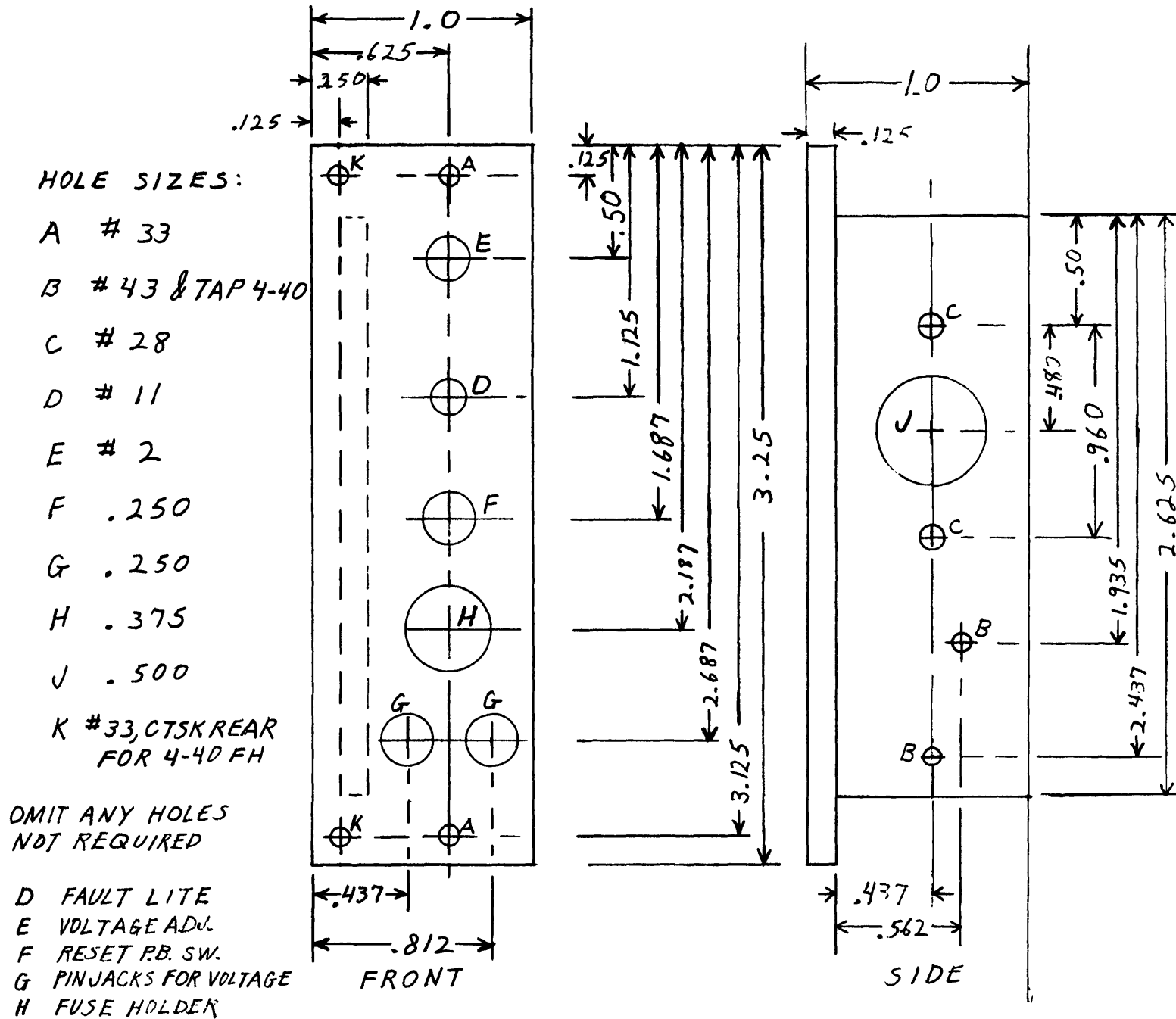

Figure 12 — Overvoltage Protection Card Layout





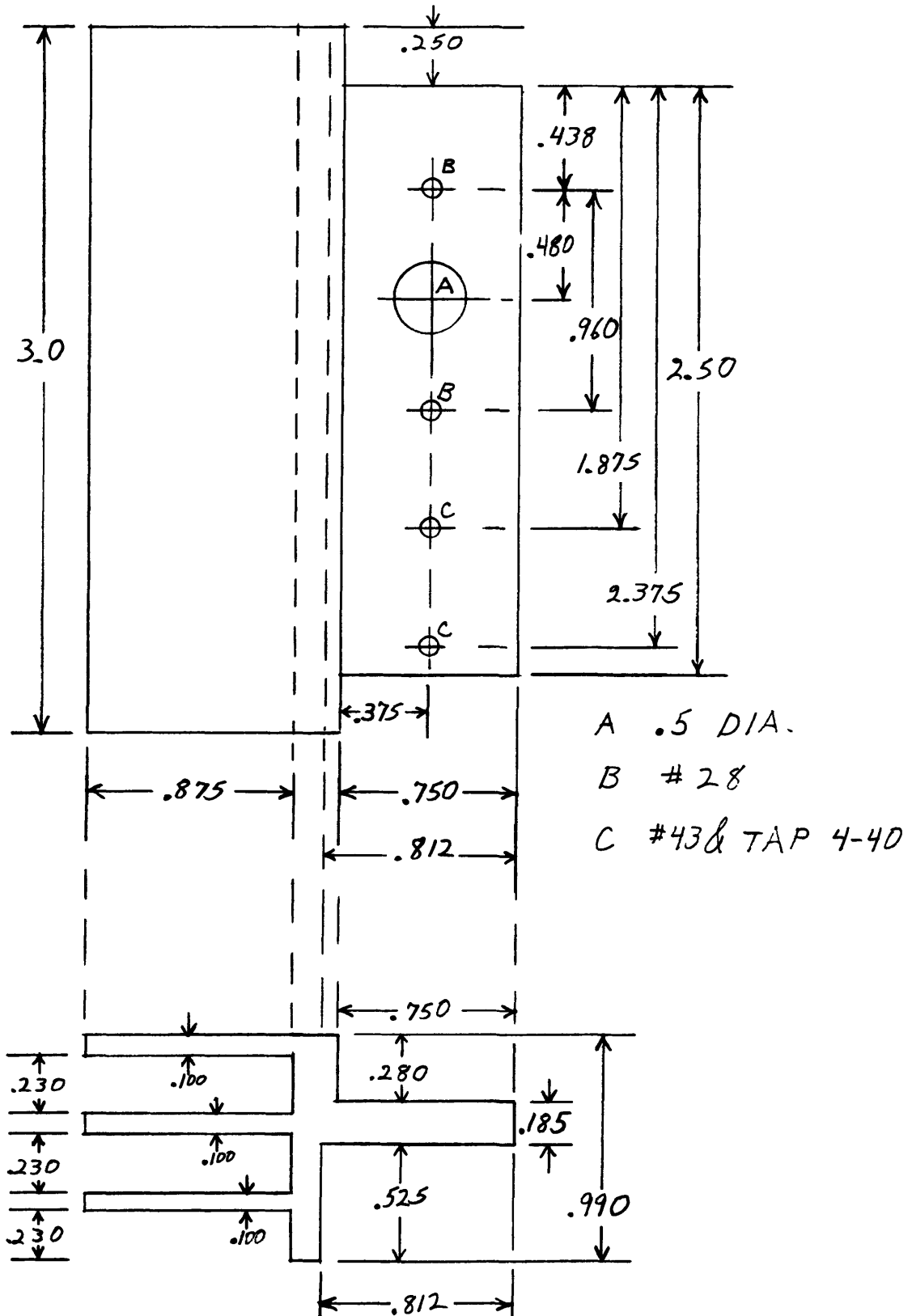


Figure 14 - 13 W Heatsink for Regulator Card

HOLE SIZES:

A #33, CTSK REAR FOR 4-40 FH

B #33

C #43, TAP 4-40

D #36, TAP 6-32

E #2

F .250

G .375

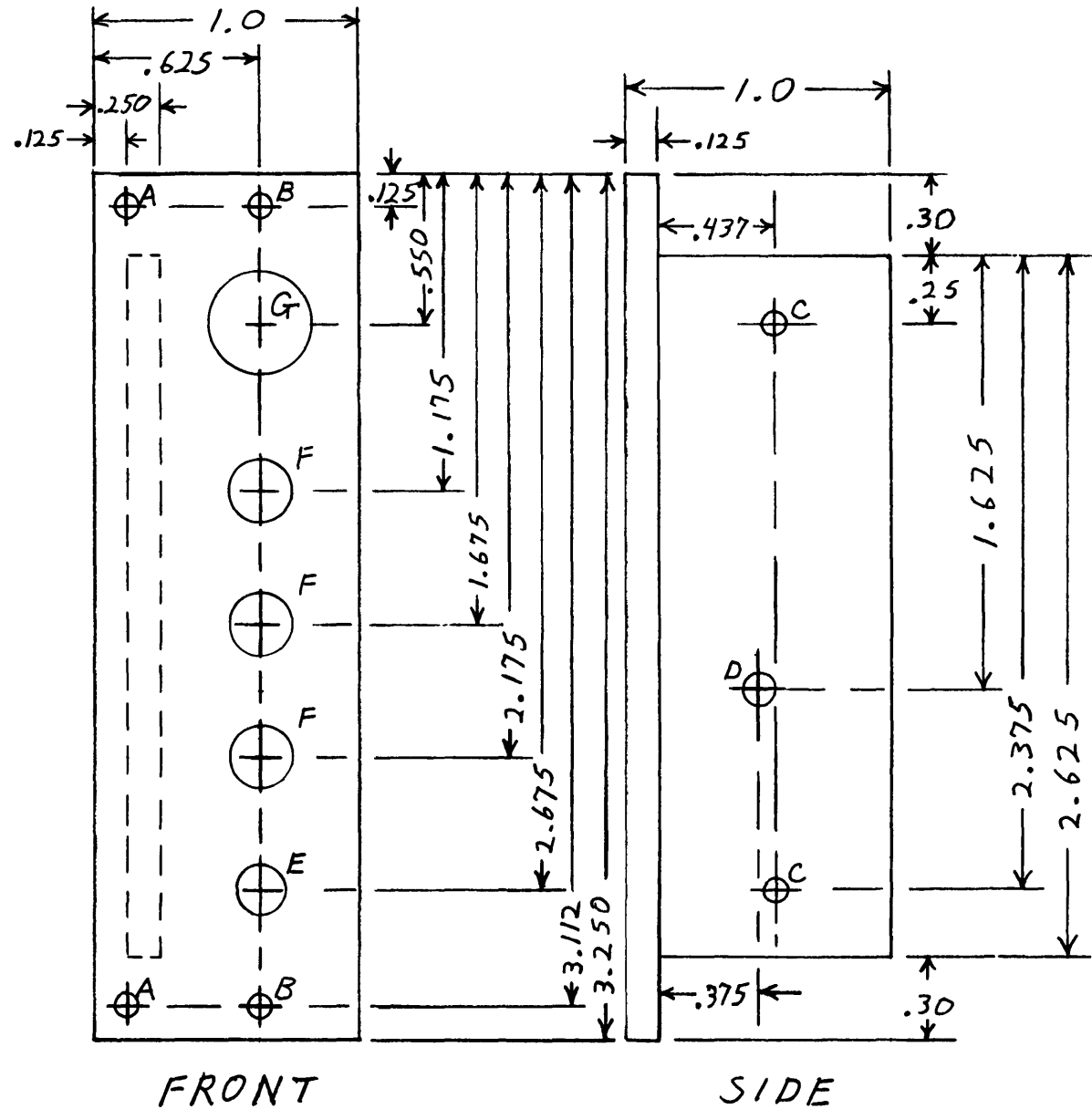


Figure 15 - Heatsink/Panel for Overvoltage Protection Card