

March 24, 1958

NATIONAL RADIO ASTRONOMY OBSERVATORY

TECHNICAL NOTE NO. 1

Low Noise Pre-Amplifiers for Radio Astronomy

by

Dr. J.W. Findlay

National Radio Astronomy Observatory  
Green Bank, West Virginia

March 24, 1958

National Radio Astronomy Observatory - Technical Note No. 1

Low Noise Pre-Amplifiers for Radio Astronomy

Summary

A brief theoretical and practical description is given of the principles of design and construction of low noise IF amplifiers, operating on a frequency of 30 Mc/s, suitable for use in radio astronomy.

1. Introduction

A very important branch of radio astronomy requires that good receivers, of high sensitivity, low noise and flat bandwidth be used in the range of frequencies between 1000 Mc/s and 1425 Mc/s. The need for low noise receivers in this range is still met best by using a crystal mixer followed by an intermediate frequency amplifier. The noise figure (referred to as NF) of such a receiver is determined by the noise generated in the crystal mixer, the mixer loss and by the noise figure of the IF amplifier.

This note describes the theory and practice of constructing an IF amplifier of low NF. This is best achieved by making what is called a "pre-amplifier". This is a small IF amplifier which is normally an integral unit with the mixer. The IF signal from the pre-amplifier is sent by RF cable to the receiver proper. The pre-amplifier should have more than enough gain to overcome the cable losses.

The requirements for a good pre-amplifier may be summarized:

- (a) It should give, when properly matched to the crystal mixer, the lowest possible NF for the

mixer - pre-amplifier combination over as wide a range of frequencies as possible.

- (b) The pre-amplifier band-pass characteristic should, in many requirements, be very flat.
- (c) The stability of the gain and band-pass of the pre-amplifier should be good.

## 2. Design considerations for pre-amplifiers

The pre-amplifier, although contributing only a relatively small part to the NF of the mixer - pre-amplifier combination, can and should be designed in the best possible way. This choice of design requires decisions on the following points:

- (a) What is the best pre-amplifier circuit design?
- (b) What tubes give the best performance?
- (c) The various components in the circuit which influence the NF should be known and chosen to minimize the NF.
- (d) The way of achieving the best match for low NF between the mixer and pre-amplifier must be understood.
- (e) The band-pass of the pre-amplifier may have to be wide and flat and the NF must still be low. This requires special design.
- (f) The ways for stabilizing gain and band-pass of the pre-amplifier must be known.

This present note covers the design points (a) (b) (c) and (d). The two points (e) and (f) are somewhat linked with

the other four, and these will be considered in a subsequent note. The work described is first a theoretical study of low noise pre-amplifiers, and second a description of the details of design and construction of such a pre-amplifier. The practical part of this work was not designed to develop the lowest possible NF, but rather to determine how the critical components in such a pre-amplifier may be designed, constructed and, in practice, adjusted.

Paragraph 3 outlines all the essential theory and Paragraph 4 gives practical design results and the results of measurements on a pre-amplifier. For convenience, an IF of 30 Mc/s has been considered throughout.

### 3. The theory of low noise pre-amplifiers.

Most of the following theory is derived from the book "Vacuum Tube Amplifiers" by Valley and Wallman - Volume 18 of the Radiation Laboratory Series. This will be referred to as V&W. The theory is only reproduced here in order to select the most important results for easy reference. Equations in this note will be referenced by their numbers in V&W.

#### (a) Choice of the best pre-amplifier circuit

This is considered in great detail in V&W (see pages 643-666). The conclusion reached at page 656-7 is that the best circuit is a grounded cathode neutralized triode input stage followed by a grounded grid triode stage. This solution, reached by 1948, still seems to be valid in practice, since all the available low-noise pre-amplifiers (known to the author) still use the same basic circuit.

V1-6AK5

V2-6AK5

V3-6AK5

V4-6AK5

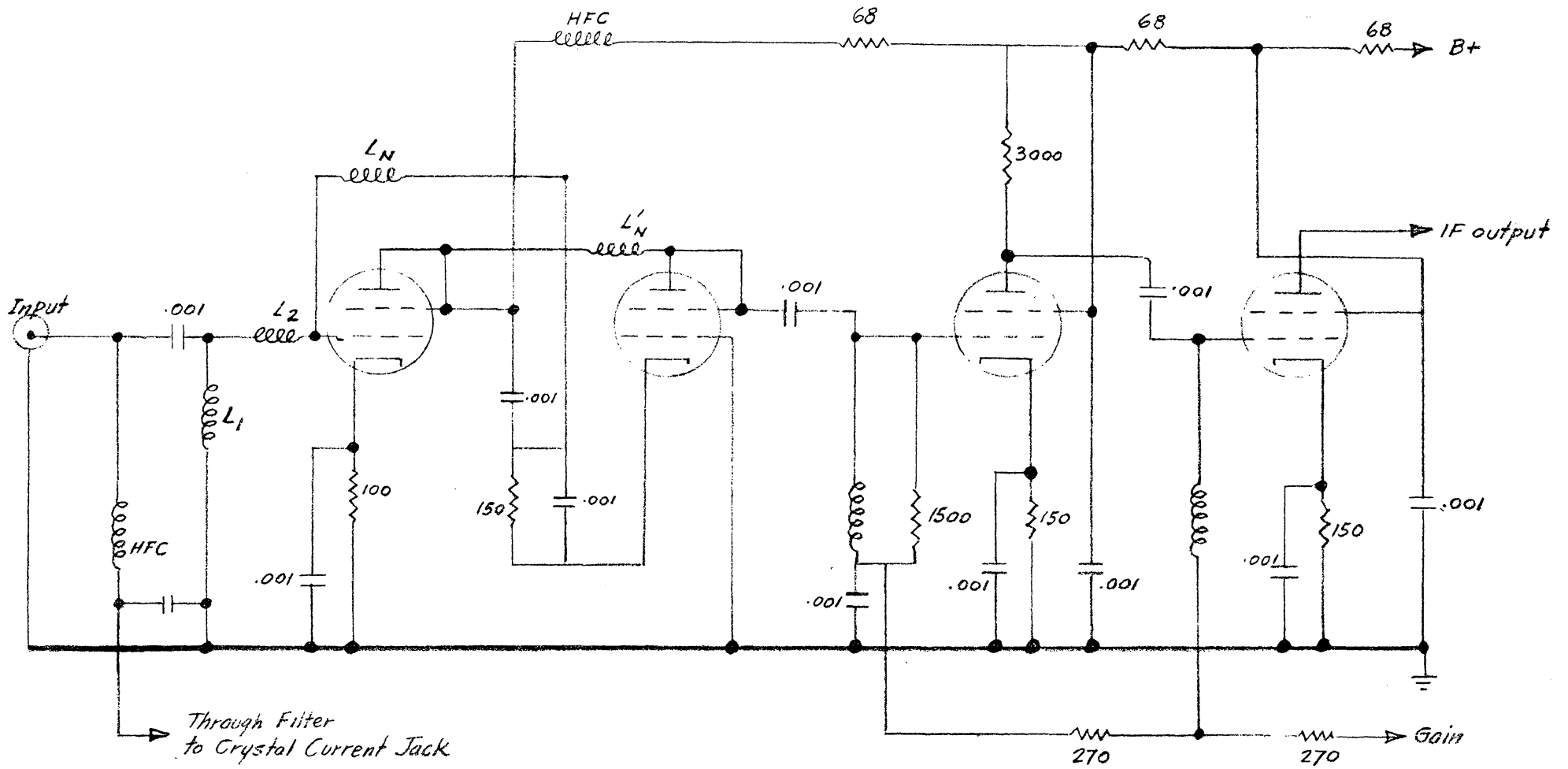


FIGURE 1

Circuit of a grounded-cathode-triode grounded-grid-triode pre-amplifier.

V<sub>1</sub> - 6AK5

V<sub>2</sub> - 6J6

V<sub>3</sub> - 6AK5

V<sub>4</sub> - 6AK5

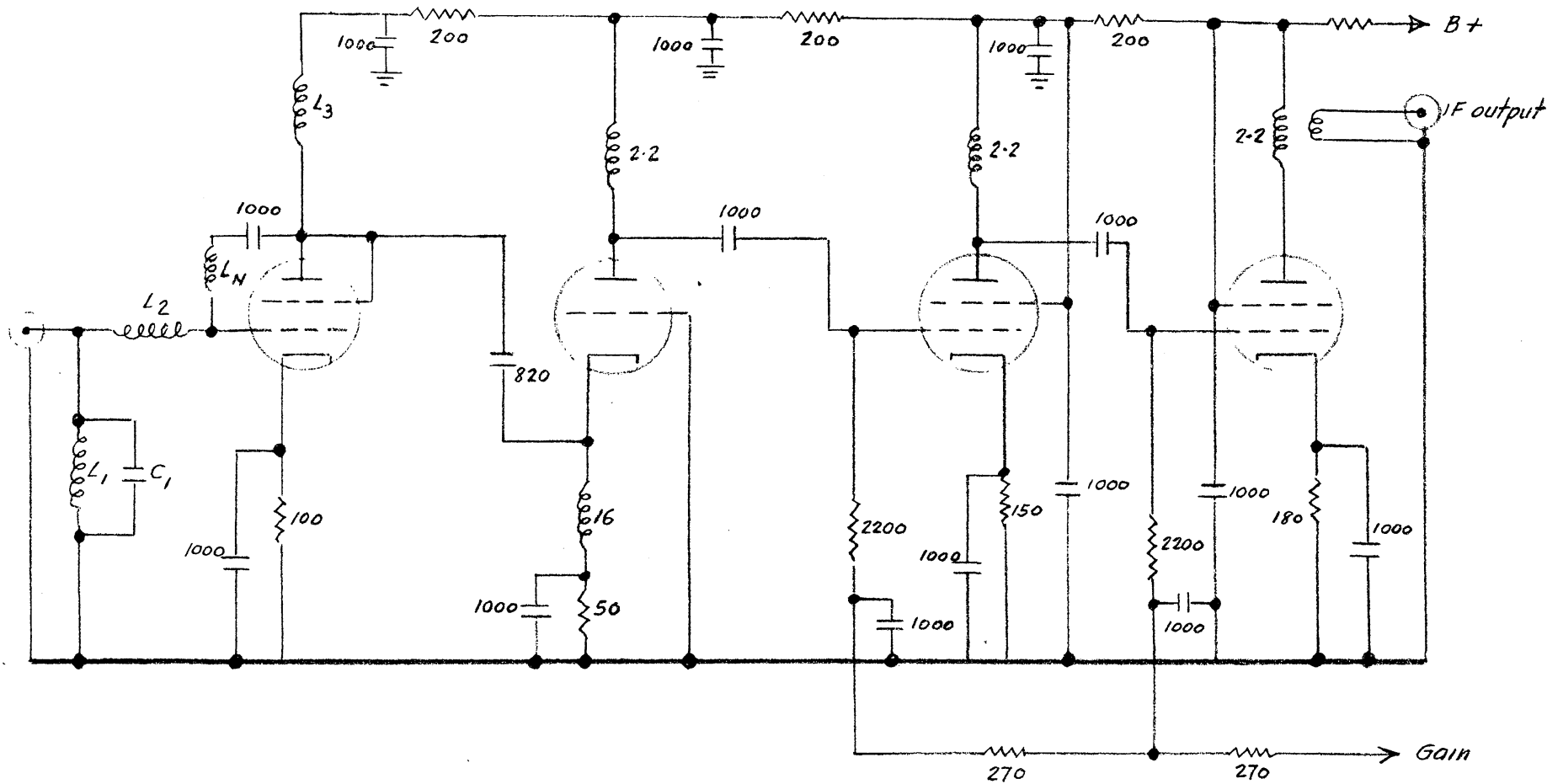


FIGURE 2

Circuit of experimental pre-amplifier used for testing.

The NF of this pre-amplifier is almost completely determined by the NF of the first stage. This stage is very stable, and the amplifier is comparatively simple to design and adjust.

An example of such a circuit is given in Figure 1, which is a copy of V&W figure 13.13 on page 661.

This circuit is not completely typical of the best practice. V&W admit that V2 would have better been a 6J6. This would avoid the need to neutralize the cathode-plate capacity of V2, which is high in a 6AK5, and so  $L_N$  would not be needed. V&W quote an average NF of 1.6 db for the circuit of Figure 1 in production.

In the present work a circuit very similar to Figure 1 was used. The final form of this circuit is shown in Figure 2.

#### (b) Choice of the best tube type

The choice of tubes is quite critical for both V1 and V2, since this pair determines the overall NF of the pre-amplifier. For V1 a large transconductance ( $g_m$ ) and a small inherent noise are important. Unfortunately, there seems to be no adequate theory (none is known to the author) for choosing the best tube. As will be shown later, the tube noise is approximately minimized by having a large  $g_m$  (see equation (3)) and a small value of the grid cathode conductance due to transit-time effects. (See equation (1)) Equation (1) also shows that a small value of B is desirable. There seems to be no way of determining B except by measurement.

As a guide to current practice, Table I shows the tubes used in a few typical pre-amplifiers.

Table I. Some typical 30 Mc/s pre-amplifiers

Pre-amplifier	$V_1$	$V_2$	Remarks
V&W page 661 Figure 1 of this note	6AK5-Triode connected	6AK5-Triode connected	V&W admit a 6J6 would be a better choice for $V_2$ . Mean NF was 1.6db
LEL pre-amplifier	6BC4-Triode connected	6CB6-Triode connected	NF measured is about 1.85 db with a 3 db bandwidth of 7 Mc/s
AIL Type 13130 pre-amplifier	404 A-Triode connected	417A	NF about 1.5 db deduced from per- formance with Empire Devices Mixer at 1400 mc
Experimental pre- amplifier used for present work	6AK5-Triode connected	6J6	NF of 1.8 achieved with a 3 db band- width of 3 Mc/s

(c) The theory of a minimum NF circuit

This theory is dealt with fully in Chapter 13 of V&W. Only the salient points will be collected here.

(i) The equivalent noise representation of the first tube

Figure 3 shows the equivalent noise representation of a triode. Sources of noise represented by generators  $i_p$  and  $i_g$  ex-



ist in the tube due to the fluctuations in the flow of electrons. Expressions for  $i_p$  and  $i_g$  are given in V&W, equations 13.15 and 13.16:

$$\overline{i_g^2} df = 4 RB TG_t df \text{ (1) (V\&W 13:15)}$$

Where  $G_T$  is the grid-cathode conductance due to transit time loading, B is a factor of about 5, k is Boltzmann's constant and T is room temperature in degrees K.

$I_p$  is conveniently regarded as being equivalent to the thermal noise in a conductance  $R_{eq} G_m^2$  in the anode-cathode circuit, or, as is equivalent, to the noise in a resistance  $R_y$  in the grid-cathode circuit.  $R_{eq}$  is then known as the equivalent noise resistor, and equation (1) may be written:

$$\overline{i_p^2} df = 4 RT R_{eq} G_m^2 df \text{ (2) (V\&W 13:16)}$$

It is possible to calculate  $R_{eq}$  for a triode, since approximately

$$R_{eq} = \frac{2.5}{G_m} \text{ (3) (V\&W 13:17c)}$$

However, agreement between calculated and observed values of  $R_{eq}$  is not good for most tubes, although the value calculated for a 6AK5 (with a  $G_m$  of 6700 micro-mhos), of 380 ohms, is quite a good practical figure.

(ii) Other sources of noise in the circuit of  $V_1$

In (i) above we have written down the noise contributions from the tube itself. In addition noise arises from con-

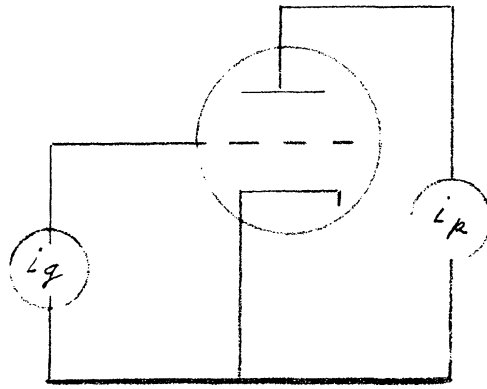


FIGURE 3 - The equivalent noise representation of a triode

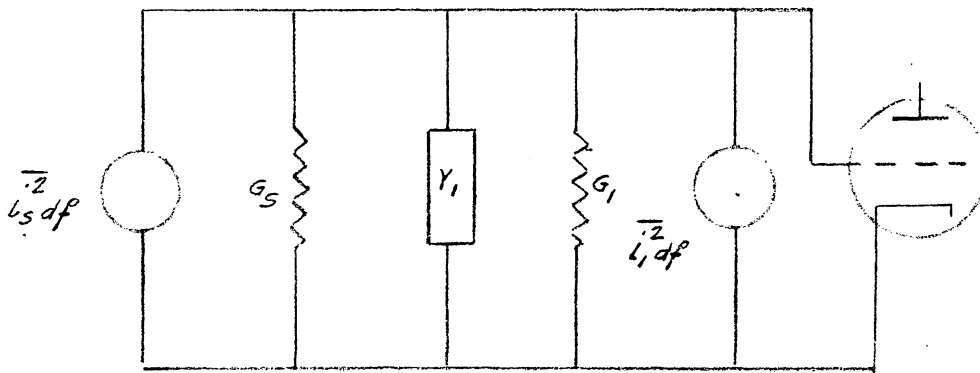


FIGURE 4 - Equivalent circuit for input network

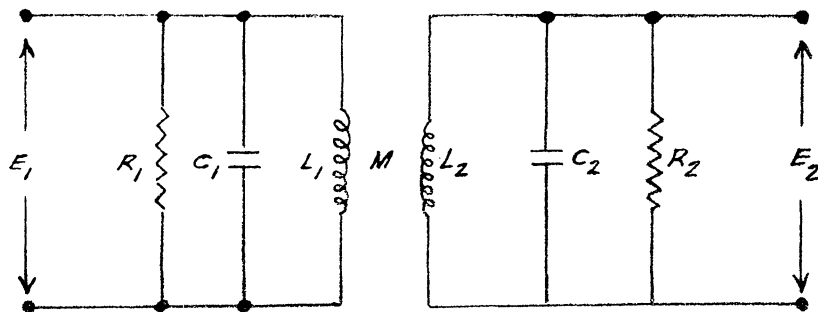


FIGURE 5 Inductance - coupled - double-tuned circuit.

ductances connected to the input of  $V_1$ . Figure 4, which is V&W Figure 13.2, shows what these noise sources are. In Figure 4

$G_s$  is the transformed value of the source conductance which appears across the input of  $V_1$ .  $G_1$  represents the network ohmic losses across the input of  $V_1$ .  $Y_1$  is the total susceptance across the input of  $V_1$ . Thus the total admittance presented to the input of  $V_1$  is

$$Y_s = G_s + G_1 + j Y_1 \quad (4) \quad (V\&W \ 13 \ X_{19})$$

(iii) Minimizing the NF

The first step in the theory of minimizing the NF is to obtain an expression for the NF itself. The NF for the first stage is found by dividing the total noise power at the tube output by the noise power arising from a thermal noise generator of conductance equal to the transformed source conductance  $G_s$ . Thus, V&W add the two thermal noise generators which exist at the input of  $V_1$ :

$$\left. \begin{aligned} \overline{i_s^2} \, df &= 4kTG_s \, df \dots \\ \overline{i_s^2} \, df &= 4kTG_1 \, df \dots \end{aligned} \right\} (5) \quad V\&W \ 13.10$$

(Note - V&W include a factor  $\alpha$  in the second of these expressions. With the input losses due to pure resistance at room temperature  $\alpha = 1$ ).

Using equations (1), (2) and (5) V&W derive an important expression for the Noise Factor of the first stage ( $F_1$ ).

$$F_1 = 1 + \frac{G_1}{G_s} + \frac{B_{GT}}{G_s} + \frac{R_{oq} | Y_s + G_t |^2}{G_s} \dots (6) \quad \text{V\&W 13.52}$$

This equation is useful, for from it we can derive several important rules for getting a low NF and also we can find the best value of  $G_s$  to use for a minimum NF. To find the best value of  $G_s$ , the transformed source admittance, the expression for  $F_1$  is differentiated and  $\frac{\Delta F_1}{\Delta G_s}$  set = 0. Then, after some approximations, two simple results emerge:

$$G_s \text{ opt} = \frac{\sqrt{G_{Bl}}}{R_{oq}} \dots (7) \quad \text{(V\&W 13.58)}$$

$$F_1 \text{ opt} = 1 + 2 \sqrt{G_{Bl} R_{oq}} \dots (8) \quad \text{(V\&W 13.59)}$$

where  $G_{Bl} = G_1 + G_T$   $1 \text{ o} = \frac{G_1 + B_{GT}}{G_{Bl}} \dots (9) \quad \text{(V\&W 13.56)}$

Equation (7) is very useful since it defines the best admittance that the source should present to the input of  $V_1$  for the lowest noise figure.  $F_1 \text{ opt}$  is the lowest possible noise figure achievable.

This can all be made easier by an example.

Example 1

Take the case of a 6AK5 used as a triode for  $V_1$ . The source is to be a crystal mixer, of 300 ohms resistance, and with a shunt capacity of 40  $\mu\text{f}$ .

First, determine  $G_1$  and  $G_T$  for the 6AK5.  $G_1$  is the conductance of the total network losses at the input of  $V_1$ . Suppose the input circuit has a Q of 150 and a capacity  $C_s$  of 10  $\mu\text{f}$ , then  $G_1$  is given by

$$G_1 = \frac{2 \pi f C_s}{Q} \dots (10) \quad \text{(V\&W 13.47)}$$

and so in our example  $G_1 = 12 \mu \text{ mhos}$  at 30 Mc/s.

$G_t$  is the conductance of the tube input due to transit time damping. It is not well determined for any tube. For a 6AK5 at 30 Mc/s V&W (page 638) say it is about 12  $\mu \text{ mhos}$  and that B is about 5.

Hence, from the equation (9),  $G_{B1} = 24 \mu \text{ mhos}$  and, taking  $B = 5$ ,  $c$  is found to be 3.

Now in equation (7) use the value of  $R_{eq}$  from (3) and get  $G_s \text{ opt} = 435 \mu \text{ mhos}$ .

That is, the optimum transformed resistance that the source of 300 ohms should present to the input of  $V_1$  is  $\frac{106}{435} = 2300$  ohms.

The same values put into equation (8) show that the best value of noise figure for the first stage only will be

$$F_1 \text{ opt} = 1.24 \text{ db}$$

To sum up this theory of minimum noise figures, let us look again at equation (6), (7) and (8).

The following rules emerge for minimum noise figure:

- I. Make  $Y_1 = 0$ . That is, always tune out any reactance at the input to the first stage of the pre-amplifier.
- II. Keep  $G_1$ , the losses in the input circuit small.  $G_1$  contributes directly to  $F_1$ , but also indirectly by increasing  $Y_s$ .
- III. Present an admittance to the input of  $V_1$  as given by equation (7).

Many reasons may prevent the achievement of a 30 Mc/s NF as low as 1.24 db. Nevertheless, V&W (page 645) report a NF as low as 1.1 db and a median value of 1.35 for a very carefully built

30 Mc/s amplifier using a 6AK5 input, followed by a 6J4.

(d) The input network

(i) The theory of the network

It is necessary now to describe the theory of the design of an input circuit which will transform the source conductance to the optimum value at the tube input. For the example chosen in (c) above, this implied transforming the crystal of 300 ohms resistance to the 2300 ohms the 6AK5 would like to see in order to give a minimum NF.

This subject is treated in V&W Chapter 5. In that chapter, the properties of the double tuned interstage coupling are considered in detail. The part of this work which we need is that which deals with the circuit of Figure 5 (V&W Figure 5. 1a). This circuit is, of course, not the only one which might be used, but it, or one of its derived equivalents, proves the most useful in practice.

The only results which we need are that:

(a) It is assumed that  $L_1$  and  $C_1$  and  $L_2$  and  $C_2$  are resonant at the mid-band frequency.

(b) The driving point admittance  $Y_{11}$ , which is the ratio of Input current to Input voltage is given by

$$Y_{11} = \frac{(1 + s^2 - u^2) + j\omega r \sqrt{b + 2}}{R_1 (1 + j \frac{\omega}{Q_2/Q_1} u)} \quad (11) \quad (V\&W \ 5.23)$$

This driving point admittance is the quantity we need, since it tells us the input admittance to the network for any termination.

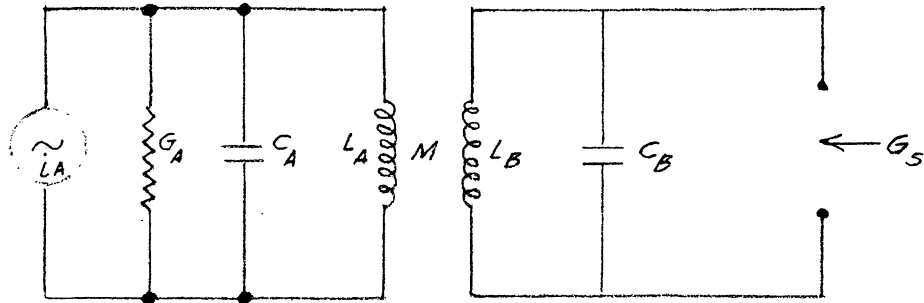


FIGURE 6 — Practical case of matching circuit

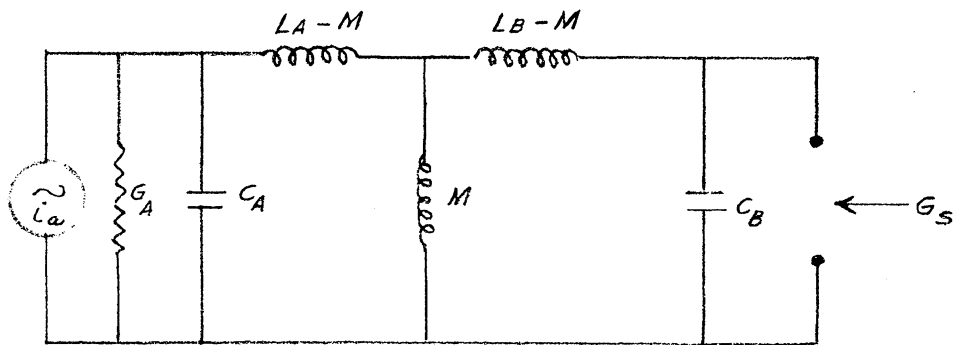


FIGURE 7 — An equivalent network to Figure 6

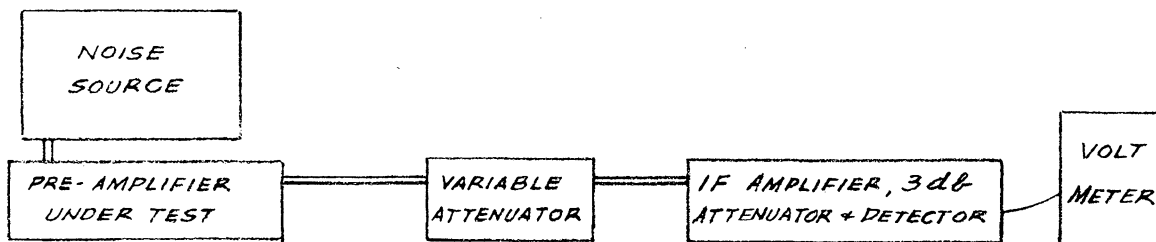


FIGURE 8 — The system used for measuring noise figure

Figure 6 shows the practical circuit we need to analyze. An expression is needed for  $G_s$ , the conductance presented to the tube, in terms of  $G_a$ . Equation 11 is simplified when we are concerned only with the mid-band frequency  $f_0$  and the circuit of Figure 6. V&W derive the simple form for  $G_s$  as

$$G_s = \frac{K^2 Q_A^2 (C_B/C_A)}{1 + Q_A^2 \alpha^2} G_A \quad (12) \quad (V\&W \ 13.117)$$

where  $\alpha = (f/f_0 - f_0/f)$  so that the mid-band case becomes

$$G_s = K^2 Q_A^2 \left( \frac{C_B}{C_A} \right) G_A \quad (13)$$

This equation is all we need to get the source impedance correctly transformed. An example will show the method.

### Example 2

In Example 1 we showed that, for minimum NF a source resistance of 300 ohms should be transformed to 2300 ohms, or a conductance of 435  $\mu$  mhos. Thus  $G_s = 435 \mu$  mhos and  $G_a = \frac{10^6}{300} = 3333 \mu$  mhos

Use (13) and get

$$\frac{G_s}{G_a} = K^2 Q_A^2 \frac{C_B}{C_A} = \frac{435}{3333} = 0.130$$

If we follow Example 1, we see that  $C_A$  and  $C_B$  are both fixed, since we chose the mixer capacity ( $C_A$ ) to be 40  $\mu$ pf and the tube input capacity, with strays, to be 10  $\mu$ pf.  $K^2 Q_A^2$  can be chosen, but usually the desirable choice is that the coupling should be transitional, and for this  $K^2 Q_A^2 = 1/2$ . \_\_\_\_\_ (14) (V&W 13.120)

Therefore, in the transitional coupling case Equation 13 becomes:

$$G_s = \frac{C_B}{2C_A} G_A \quad (15) \quad (V\&W \ 13.122)$$



So, for our example,  $\frac{G_S}{G_A} = \frac{C_B}{2C_A} = \frac{10}{80} = 0.125$

and we desire to have  $G_S/G_A = 0.130$

So, chiefly because we chose our mixer capacity so high, we arrive fortuitously at almost the correct value for  $G_S$ .

The rest of the design is now easy.  $L_A$  must resonate with  $C_A$  at 30 Mc/s and must therefore be 0.71  $\mu$ h, and  $L_B$  must resonate with  $C_B$  and thus in 2.84  $\mu$ h.  $M$  is got from the fact that  $K$ , the coefficient of coupling is:

$$K^2 = \frac{M^2}{L_A L_B} \quad (16)$$

and by using Equation (14).

Using (14) first we see that  $K = \frac{.707}{Q_A}$  and  $Q_A = \frac{2 \pi f_0 C_A}{G_A} = 2.26$

and hence  $K = 0.313$ . Hence  $M = \underline{0.45 \mu\text{h}}$ .

### (ii) Practical networks

The network of Figure 6 is not as easy to adjust as a T or II network. Figure 7 shows the T network which is equivalent to Figure 6. The use of such a network may be illustrated by continuing our example further. We found values for  $L_A$ ,  $L_B$  and  $M$ . Thus the three inductances in Figure 7 must be:

$$\begin{aligned} L_A - M &= \underline{0.26 \mu\text{h}} \\ M &= \underline{0.45 \mu\text{h}} \\ L_B - M &= \underline{2.39 \mu\text{h}} \end{aligned}$$

A still further simplification may in some cases be possible in practice; to omit  $L_A - M$ , since it is nearly zero. We should have to increase  $M$  to 0.71  $\mu$ h, so that  $L_A - M$  is zero and  $L_A$  still resonates with  $C_A$ . We have also to alter  $L_B - M$  to 2.13  $\mu$ h so that

$L_B$  still resonates with  $C_B$ . The only changes that result are as follows:

From equation (16)  $K$  is now 0.50 and so by (13):-

$$\frac{G_s}{G_A} = \underline{0.32}$$

This is perhaps too far removed from the desired value of 0.125 to represent a practical circuit for the example chosen.

#### 4. The design and construction of a 30 Mc/s pre-amplifier

The theory that has been outlined has been tested by work on a 30 Mc/s pre-amplifier. The circuit used in this pre-amplifier varied, but essentially it was that of Figure 2. The mechanical and electrical layout and construction of the pre-amplifier was not perfect, but since the experiments were intended to show how, in practice, the various elements of the circuit should be designed and adjusted, and not to produce the lowest possible NF, these shortcomings of the pre-amplifier were overlooked.

##### (a) Noise figure measurements

The system for measuring NF is shown in Figure 8. The post-amplifier used had a built-in 3db attenuator, and a pass-band about 10 Mc/s wide at the 3 db points. The noise generator was a noise diode with a 300 ohm load. The impedance of this source and its connector was measured at 30 Mc/s to be a resistance of 300 ohms with 12  $\mu$ f in parallel. Since the pre-amplifier might eventually be used with a mixer of 40  $\mu$ f capacity, a further 25  $\mu$ f was added across  $L_1$  ( $C_1$  in figure 2) so that the input circuit would be correctly designed for such a mixer.

The absolute values for NF measured are probably good to 0.2 db, but the relative values are, of course, much more accurate.

Measurements were made by adjusting the variable attenuator until the noise output was an easily read value. The extra 3 db of attenuation was switched in and the noise source current increased from zero until the original noise output was again achieved. If  $i$  milliampers is the diode current when this occurs, the NF is given by:

$$NF = 10 \log_{10} \frac{1}{i} \quad (17)$$

(b) First stage gain

A simple qualitative example was noted of the importance of high gain in the first stage. As originally built the pre-amplifier had a rather low gain, due to improper tube bias. The measured NF was 5.0 db. Correction of the bias and coupling condensers (which were rather small) improved this figure to 3 db.

(c) Input coupling network

A coupling network calculated very much along the lines of Example 1 was first designed. As will be described under paragraph on "neutralizing", there is considerable difficulty in adjusting such a network together with  $L_N$  and  $L_3$  (all references are to Figure 2). Eventually, the input network used was that sketched in Figure 2.  $L_1$  and  $L_2$  had the following values

$$L_1 = 0.68 \mu\text{h}$$

$$L_2 = 4.5 \mu\text{h}$$

The calculated ratio of  $G_s/G_A$  for these values is 0.089, which is about 30% smaller than is desirable. Nevertheless, the effect on

NF should not be great, and in fact, using V&W Figure 13.7 suggests it will be only about 0.02 db.

The Q of the coils used for  $L_1$  and  $L_2$  was not very high. For ease of experiment, slug-tuned inductors were used. The measured Q's were about 90. An unsuccessful attempt was made to detect the change in NF consequent on using coils of Q about 150, and in fact a consideration of Equation 6 suggests that such an effect would not be found until the NF was considerably less than the 1.8 db achieved.

(d) The neutralizing coil

The purpose of  $L_N$  is to neutralize the grid-anode capacity of  $V_1$ . This capacity is about 1.2  $\mu\text{f}$ , so that  $L_N$  should be about 24  $\mu\text{h}$ . However, stray capacities can easily alter this value, and so a way of adjusting  $L_N$  has to be found. One way is to disconnect one of the heater connections from  $V_1$ , thus leaving that tube cold. A signal fed to the input of the pre-amplifier can only reach the output via the grid-anode capacity of  $V_1$ . Thus,  $L_N$  may be adjusted by connecting a 30 Mc/s signal source to the amplifier input and tuning  $L_N$  for minimum output.

This system was adopted, and proved to work. Nevertheless, such an adjustment of  $L_N$  leads to several difficulties. Both  $L_3$  and  $L_2$  should be adjusted for resonance. Changes in  $L_N$  are reflected, by Miller effect, into the grid-cathode circuit to change the reactance across  $L_2$ . Changes in  $L_3$  also effect the values of these reactances. Also, it is difficult to use a slug-tuned adjustable  $L_N$ , since stray capacities may affect the value of  $L_N$  at

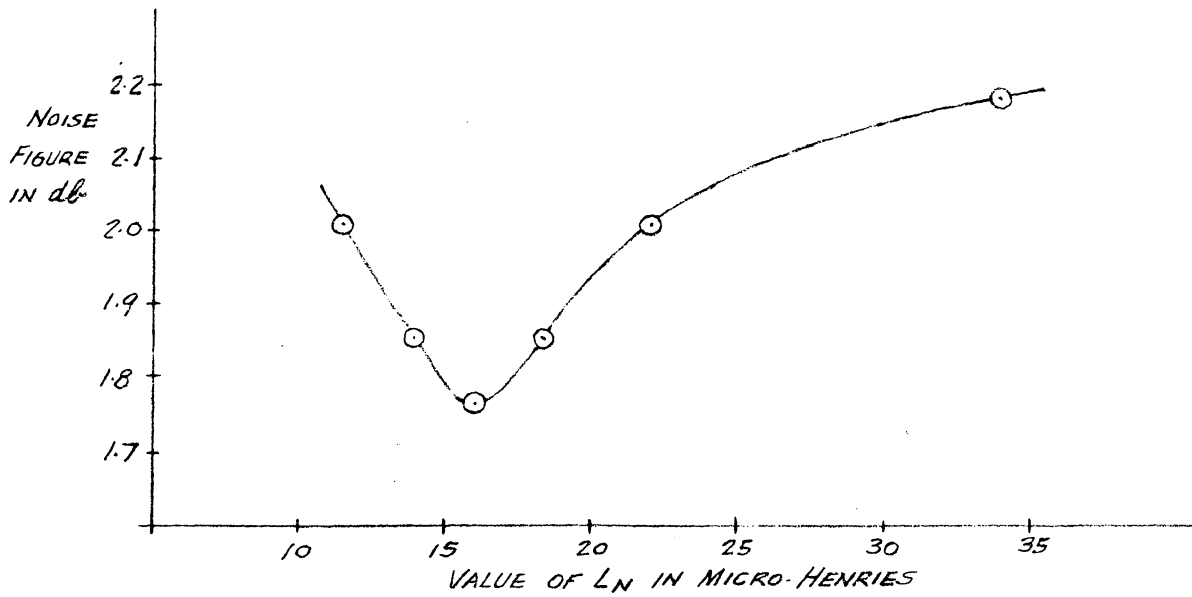


FIGURE 9 — The effect on NOISE figure of the size of the neutralizing coil.

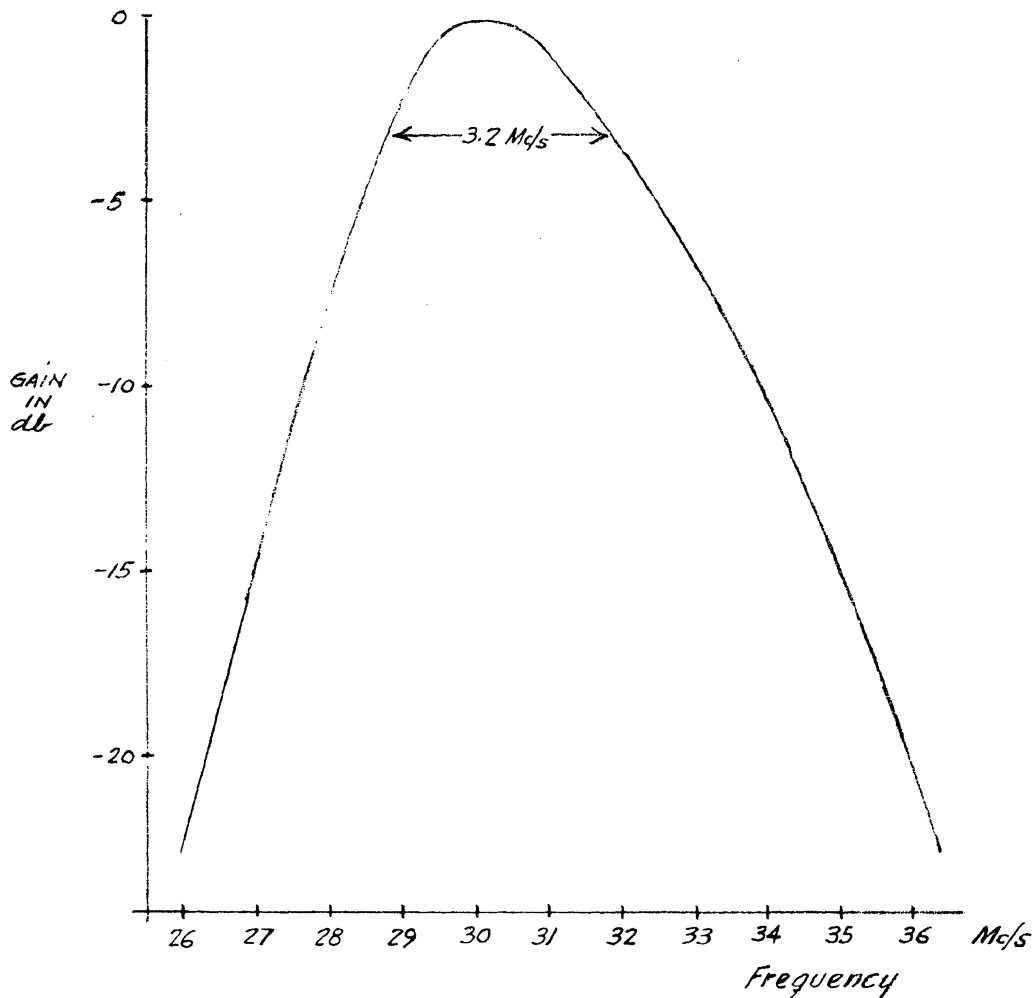


FIGURE 10 — Band-pass characteristic of the experimental pre-amplifier

resonance. For example - using a slug-tuned  $L_N$  suspended in the wiring led to a value of  $L_N$  at resonance of about 10.5  $\mu\text{H}$ . The value found for an  $L_N$  of a simple coil type was 16  $\mu\text{H}$ . The difference arose from the stray capacities due to the slug-tuning.

After some experimenting, a good way for adjusting  $L_N$  was found. First, an adjustment of  $L_3$  was needed. This could be made by removing  $V_2$  from its socket. With  $V_2$  in place,  $L_3$  is highly damped and resonance is hard to detect.  $L_3$  can be adjusted accurately enough with  $V_2$  absent. Alternatively,  $L_3$  may be replaced without serious loss of NF by a radio-frequency choke.

Then  $L_1$  is adjusted to be resonant with the input capacity to 30 Mc/s ( $L_2$  is of course disconnected from  $L_1$  for the check).  $L_2$  is reconnected and  $L_N$  is then altered over a range of values and the NF measured for each value.  $L_2$  is adjusted to resonance for each value of  $L_N$ . This is essential, since for best NF  $L_2$  must be resonant and changes in  $L_N$  are reflected across  $L_2$  by Miller effect and thus alter the tuning of  $L_2$ .

Such a test was made, and the results are shown in Figure 9. Various coils were made for  $L_N$ , varying from 11.5  $\mu\text{H}$  to 34  $\mu\text{H}$ . These coils all had Q's of between 50 and 80. They were used in turn, in the circuit of Figure 2.  $L_3$  was a 16  $\mu\text{H}$  choke and  $L_2$  was adjusted each time for resonance.

Figure 9 shows a marked dip in NF at  $L_N = 16 \mu\text{H}$ , a result which confirms both the resonant value of  $L_N$  and also the improvement in NF consequent on good neutralizing.

Lastly, a note on the Q of  $L_N$  should be made.  $L_N$  can contribute, by its losses, to the NF, and so its Q should be reasonably

high. V&W on page 649 state that the contribution of the conductance  $G_N$  of  $L_N$  to the NF is given by  $G_N/G_S$ . In our present case  $G_S = 435 \mu\text{mhos}$ .  $G_N$  may be related to the  $Q_N$  of  $L_N$  by

$$G_N = \frac{1}{2 \pi f_0 Q_N L_N}$$

and so  $G_N = 3.3 \mu\text{ mhos}$  for  $Q_N = 100$ . Hence there is going to be a very small contribution to the NF, of the order of less than 1% in power ratio, due to an  $L_N$  which has a Q of about 100.

(e) The band-pass characteristics

No attempt was made to broaden or flatten the pass-band of the pre-amplifier. The pass-band used is shown in Figure 10.

(f) Varying tube characteristics

The following Table II shows the effects of using a number of different tubes in the pre-amplifier. The 6AK5 ( $V_1$ ) was altered first. The results for changing 6J6's were taken with the best 6AK5 (marked \*) as  $V_1$ . The results show, as would be expected, that the tube used as  $V_1$  is of greatest importance. They also show that the contribution from  $V_2$  to the NF is very small, since the NF hardly varies with changing tubes in  $V_2$ .

Table II. The effect of changing tubes on NF

Tube type	Position	Number	Manufacturer	Noise Figure db
6AK5	V <sub>1</sub>	1	RCA	2.10
		2	"	2.25
		3	"	2.33
		4	"	2.68
		5*	WE	1.85
		6	"	2.01
		7	"	1.85
		8	"	2.62
		9	TS	2.33
		10	"	2.41
		11	"	2.10
		12	"	2.18
6J6	V <sub>2</sub>	1	SO	1.85
		2	"	1.76
		3	"	1.76
		4	"	1.85
		5	"	1.85
		6	"	1.85

5. Summary

The theory and experiment reported in this note show how the first steps may be made in good pre-amplifier design. The next stage will be:

- (a) The achievement of wider bandwidths
- (b) The improvement of NF still further by careful attention to the details of design and layout and by using better tubes.